

Q5 Documentation

Boxin Zheng, Chenyuan Chu and Yitian Sun

1 Requirement 1 & 2

In this section, we will explain how we transform the $Q5_testcase.v$ into $result_5.v$, a circuit without oscillation while having the same output with the original circuit when the input does not cause oscillation in the original circuit.

1.1 Step 1: Analysis of the Case

$Q5_testcase.v$ is a circuit with 8 inputs, 14 logic gates and 6 logic loops, whose graph is shown in figure 1.

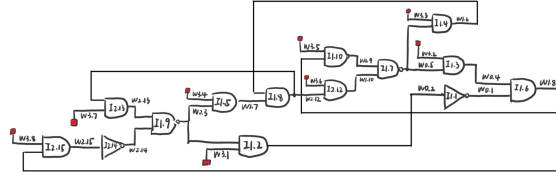


Figure 1: Circuit

Among the 6 loops, there are 4 negative loops that may cause oscillation, which are named $Loop1 - Loop4$ and drawn in deep blue, yellow, purple and red respectively. They are shown in figure 2, whose wires are listed below.

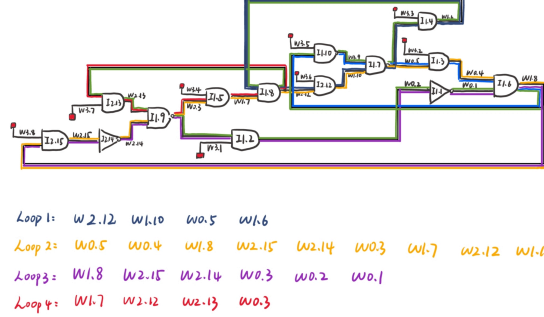


Figure 2: Loops

Given the graph above, we come up with a simple and intuitive idea: we can cut off some wires to destruct positive loops so that oscillation will never occur; but meanwhile, these wires we cut off serve as the inputs of other gates g_1, g_2, \dots, g_m , so we must use something to replace them. Fortunately, it is obvious that when the input does not cause oscillation in the original circuit, each wire can be described as a logic function of input wires, like $F(I_1, I_2, \dots, I_n)$, here n is the number of input wires and $I_i (i = 1, 2, \dots, n)$ is their names. These logic functions can take the role of inputs for gates g_1, g_2, \dots, g_m , and via this method we can guarantee the new circuit's function is the same as the original one. Similarly, the *OscFlag* signal can be described as a logic function of input wires as well.

To realize this idea, we must conduct simulation with Verisim first.

1.2 Step 2: Simulation with Verisim

To begin with, we conduct simulation on the original circuit. Apparently, there are some inputs causing oscillation, which will force the simulation to abort. But as long as we change the initial input to this oscillating state, Verisim will output oscillating results in consecutive states. In the example below, Verisim senses the oscillation in input [00110100], so it just stop at the [11010100] state:

Figure 3: Stop at Oscillation Point

```

1 initial begin
2     $deposit(I0.w_002_013, 1'b1);
3     r1 = 1'b0;
4     r2 = 1'b0;
5     r3 = 1'b1;
6     r4 = 1'b1;
7     r5 = 1'b0;
8     r6 = 1'b1;
9     r7 = 1'b0;
10    r8 = 1'b0;
11    $monitor("Time=%-3t, Signals: [%b %b %b %b %b %b %b %b %b] [%b %b %b %b %b %b %b %b %b] %b",
12             $time,
13             w_003_001, w_003_002, w_003_003,
14             w_003_004, w_003_005, w_003_006,
15             w_003_007, w_003_008,
16             I0.w_000_001, I0.w_000_002, I0.w_000_003,
17             I0.w_000_004, I0.w_000_005,
18             I0.w_001_006, I0.w_001_007, I0.w_001_008,
19             I0.w_001_009, I0.w_001_010,
20             I0.w_002_012, I0.w_002_013, I0.w_002_014,
21             I0.w_002_015);
22 end

```

```
16      #260;
17      $finish ;
18  end
```

In this way, we can obtain the result of simulation when oscillation occurs

```
Time= 0, Signals: [0 0 1 1 0 1 0 0] [1 0 1 0 x x 1 0 1 x x 0 1 0]
Time= 1, Signals: [1 0 1 1 0 1 0 0] [0 1 1 0 x x 1 0 1 x x 0 1 0]
Time= 2, Signals: [0 1 1 1 0 1 0 0] [1 0 1 x x x 1 x 1 x x 0 1 0]
Time= 3, Signals: [1 1 1 1 0 1 0 0] [0 1 1 x x x 1 0 1 x x 0 1 0]
```

Figure 4: Result

Here, "x" indicate the oscillating signal, and we can find Verisim stops w switch from the oscillatory input to non-oscillatory input. So we should cha the initial input once again to proceed simulation:

```

1 initial begin
2     $deposit(I0.w_002_013, 1'b1);
3     r1 = 1'b0;
4     r2 = 1'b0;
5     r3 = 1'b0;
6     r4 = 1'b0;
7     r5 = 1'b1;
8     r6 = 1'b1;
9     r7 = 1'b0;
10    r8 = 1'b0;
11    $monitor("Time=%-3t, Signals: [%b %b %b %b %b %b %b %b  

        b] [%b %b %b %b %b %b %b %b %b %b %b %b %b %b]",  

        $time,  

12            w_003_001, w_003_002, w_003_003,  

                w_003_004, w_003_005, w_003_006,  

                w_003_007, w_003_008,  

13    I0.w_000_001, I0.w_000_002, I0.w_000_003,  

                I0.w_000_004, I0.w_000_005,  

14    I0.w_001_006, I0.w_001_007, I0.w_001_008,  

                I0.w_001_009, I0.w_001_010,  

15    I0.w_002_012, I0.w_002_013, I0.w_002_014,  

                I0.w_002_015);
16    #260;
17    $finish;
18 end

```

We can obtain the result:

```

Time= 0, Signals: [0 0 0 0 1 1 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 1, Signals: [1 0 0 0 1 1 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 2, Signals: [0 1 0 0 1 1 0 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0]
Time= 3, Signals: [1 1 0 0 1 1 0 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
Time= 4, Signals: [0 0 1 0 1 1 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 5, Signals: [1 0 1 0 1 1 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 6, Signals: [0 1 1 0 1 1 0 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0]
Time= 7, Signals: [1 1 1 0 1 1 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
Time= 8, Signals: [0 0 0 1 1 1 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 9, Signals: [1 0 0 1 1 1 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 10, Signals: [0 1 0 1 1 1 0 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0]
Time= 11, Signals: [1 1 0 1 1 1 0 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]

```

Figure 5: Result

If we keep changing the initial input to proceed simulation, we can ultimately enumerate all 2^8 inputs and their corresponding results. The complete result is attached in the appendix.

1.3 Step 3: Find the Pattern

In this step, we will explain the detailed realization of our intuitive idea: find the pattern between input pin and specific wires, and convert it to a logic function.

First and foremost, we should list the wires of the potential oscillating positive loops:

1. **Loop1:** $w_000_005, w_001_006, w_001_010, w_002_012$
2. **Loop2:** $w_000_003, w_000_004, w_000_005, w_001_007, w_001_008, w_001_010, w_002_012, w_002_014, w_002_015$
3. **Loop3:** $w_000_001, w_000_002, w_000_003, w_001_008, w_002_014, w_002_015$
4. **Loop4:** $w_000_003, w_001_007, w_002_012, w_002_013$

We observe that Loop1 and Loop4 share the wire w_002_012 , while Loop2 and Loop3 share the wire w_002_015 . That means, if we cut off these two wires and replace them with two designed logic function, we can guarantee the new circuit share the same result with the original circuit while avoid oscillation. So we will find patterns to represent these logic functions next.

1.3.1 Logic Function for w_002_012

Let's focus on the third and fourth columns of the input, as well as the fourth column from the end of the output:

```

Time= 0, Signals: [0 0 0 0 0 0] [1 0 1 0 1 0 0 0 1 0]
Time= 1, Signals: [1 0 0 0 0 0 0] [0 1 1 0 1 0 0 0 1 0]
Time= 2, Signals: [0 1 0 0 0 0 0] [1 0 1 1 1 0 0 1 1 0]
Time= 3, Signals: [1 1 0 0 0 0 0] [0 1 1 1 1 0 0 0 1 0]
Time= 4, Signals: [0 0 1 0 0 0 0] [1 0 1 0 1 1 0 0 1 0]
Time= 5, Signals: [1 0 1 0 0 0 0] [0 1 1 0 1 1 0 0 1 0]
Time= 6, Signals: [0 1 1 0 0 0 0] [1 0 1 1 1 1 0 1 1 0]
Time= 7, Signals: [1 1 1 0 0 0 0] [0 1 1 1 1 1 0 0 1 0]
Time= 8, Signals: [0 0 0 1 0 0 0] [1 0 1 0 1 0 1 0 1 0]
Time= 9, Signals: [1 0 0 1 0 0 0] [0 1 1 0 1 0 1 0 1 0]
Time= 10, Signals: [0 1 0 1 0 0 0] [1 0 1 1 1 0 1 1 1 0]
Time= 11, Signals: [1 1 0 1 0 0 0] [0 1 1 1 1 0 1 0 1 0]
Time= 12, Signals: [0 0 1 1 0 0 0] [1 0 1 0 1 1 1 0 1 0]
Time= 13, Signals: [1 0 1 1 0 0 0] [0 1 1 0 1 1 1 0 1 0]
Time= 14, Signals: [0 1 1 1 0 0 0] [1 0 1 1 1 1 1 1 1 0]
Time= 15, Signals: [1 1 1 1 0 0 0] [0 1 1 1 1 1 1 0 1 0]
Time= 16, Signals: [0 0 0 0 1 0 0] [1 0 1 0 1 0 0 0 1 0]
Time= 17, Signals: [1 0 0 0 1 0 0] [0 1 1 0 1 0 0 0 1 0]
Time= 18, Signals: [0 1 0 0 1 0 0] [1 0 1 1 1 0 0 1 0 0]
Time= 19, Signals: [1 1 0 0 1 0 0] [0 1 1 1 1 0 0 0 1 0]
Time= 20, Signals: [0 0 1 0 1 0 0] [1 0 1 0 1 1 0 0 1 0]
Time= 21, Signals: [1 0 1 0 1 0 0] [0 1 1 0 1 1 0 0 1 0]
Time= 22, Signals: [0 1 1 0 1 0 0] [1 0 1 1 1 1 0 1 0 0]
Time= 23, Signals: [1 1 1 0 1 0 0] [0 1 1 1 1 1 0 0 1 0]
Time= 24, Signals: [0 0 0 1 1 0 0] [1 0 1 0 1 0 1 0 1 0]
Time= 25, Signals: [1 0 0 1 1 0 0] [0 1 1 0 1 0 1 0 1 0]
Time= 26, Signals: [0 1 0 1 1 0 0] [1 0 1 1 1 0 1 1 0 0]
Time= 27, Signals: [1 1 0 1 1 0 0] [0 1 1 1 1 0 1 0 1 0]
Time= 28, Signals: [0 0 1 1 1 0 0] [1 0 1 0 1 1 1 0 1 0]
Time= 29, Signals: [1 0 1 1 1 0 0] [0 1 1 0 1 1 1 0 1 0]
Time= 30, Signals: [0 1 1 1 1 0 0] [1 0 1 1 1 1 1 0 1 0]
Time= 31, Signals: [1 1 1 1 1 0 0] [0 1 1 1 1 1 1 0 1 0]
Time= 32, Signals: [0 0 0 0 1 0 0] [1 0 1 0 1 0 0 0 1 0]
Time= 33, Signals: [1 0 0 0 1 0 0] [0 1 1 0 1 0 0 0 1 0]
Time= 34, Signals: [0 1 0 0 1 0 0] [1 0 1 1 1 0 0 1 1 0]
Time= 35, Signals: [1 1 0 0 1 0 0] [0 1 1 1 1 0 0 0 1 0]

```

Figure 6: Pattern of w12

Surprisingly, we can find a simple pattern between input wire w_003_003 / w_003_004 and wire w_002_012 , which can be describe as an "AND" operation. Although the result picture above displays a fraction of the whole result only, we can confirm this conclusion using the complete result in the appendix.

In Verilog, we can use a new wire named $new_w_002_012$ to replace the original w_002_012 with an elegant *assign* operation:

```

1 assign new_w_002_012 = w_003_003 & w_003_004;

```

Now w_002_012 only serves as the output of gate $I001_008$, while the $new_w_002_012$ takes on the role of the input for gate $I002_013$ and $I002_014$.

```

1 and2    I001_008(w_002_012, w_001_006, w_001_007);
2 and2    I002_013(w_002_013, w_003_007, new_w_002_012);
3 not1    I002_014(w_002_014, new_w_002_015);

```

The following picture clearly clarify the modification (the blue part):

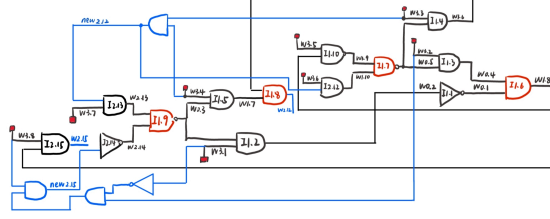


Figure 10: Modified Circuit

2 Requirement 3

In this section, we realize the function of predicting oscillation: when the input causes the original circuit to oscillate, a wire named *OscFlag* in the modified circuit will be 1, and otherwise 0.

Following the analysis in section 1, we can get similar conclusion from the result below:

```

Time= 9, Signals: [1 0 0 1 1 1 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 10, Signals: [0 1 0 1 1 1 0 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1]
Time= 11, Signals: [1 1 0 1 1 1 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
Time= 0, Signals: [0 0 1 1 1 1 0 1] [1 0 1 0 x x 1 0 1 x x 0 1 0]
Time= 1, Signals: [1 0 1 1 1 1 0 1] [0 1 1 0 x x 1 0 1 x x 0 1 0]
Time= 2, Signals: [0 1 1 1 1 1 0 1] [1 0 1 x x x 1 x x x x 0 x]
Time= 3, Signals: [1 1 1 1 1 1 0 1] [0 1 1 x x x 1 0 1 x x 0 1 0]
Time= 0, Signals: [0 0 0 0 0 0 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 1, Signals: [1 0 0 0 0 0 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 2, Signals: [0 1 0 0 0 0 1 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1]

```

Figure 11: Pattern of OscFlag (1)

```

Time= 10, Signals: [0 1 0 1 0 0 1 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1]
Time= 11, Signals: [1 1 0 1 0 0 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
Time= 0, Signals: [0 0 1 1 0 0 1 1] [1 0 x 0 1 1 x 0 1 0 x x 1 0]
Time= 1, Signals: [1 0 1 1 0 0 1 1] [x x x 0 1 1 x 0 1 0 x x 1 0]
Time= 0, Signals: [0 1 1 1 0 0 1 1] [1 0 1 1 1 1 1 1 0 1 1 0 1]
Time= 0, Signals: [1 1 1 1 0 0 1 1] [x x x 1 1 1 x x 1 0 x x x x]
Time= 0, Signals: [0 0 0 0 1 0 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 1, Signals: [1 0 0 0 1 0 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 2, Signals: [0 1 0 0 1 0 1 1] [1 0 1 1 1 0 0 1 0 0 0 0 1]

```

Figure 12: Pattern of OscFlag (2)

The conclusion can be expressed as a logic function in Verilog as follows:

```

1 assign OscFlag = w_003_003 & w_003_004 & (w_003_006 |
    w_003_007) & ~(~w_003_001 & w_003_002 & ~w_003_006 &
    w_003_007 & w_003_008);

```

Next, we add *OscFlag* to the simulation list:

```

1 initial begin
2     $deposit(I0.w_002_013, 1'b1);
3     r1 = 1'b0;

```



```

4      r2 = 1'b0;
5      r3 = 1'b0;
6      r4 = 1'b0;
7      r5 = 1'b0;
8      r6 = 1'b0;
9      r7 = 1'b0;
10     r8 = 1'b0;
11     $monitor("   Time=%-3t, Signals: [%b %b %b %b %b %b %b %b
           %b] [%b %b %b %b %b %b %b %b %b %b %b %b %b %b]
           [%b]", $time,
12           w_003_001, w_003_002, w_003_003,
           w_003_004, w_003_005, w_003_006,
           w_003_007, w_003_008,
13           IO.w_000_001, IO.w_000_002, IO.w_000_003,
           IO.w_000_004, IO.w_000_005,
14           IO.w_001_006, IO.w_001_007, IO.w_001_008,
           IO.w_001_009, IO.w_001_010,
15           IO.w_002_012, IO.w_002_013, IO.w_002_014,
           IO.w_002_015,
16           IO.OscFlag   );
17     #260;
18     $finish;
19 end

```

And we get the result like the figure below, where the last [0] or [1] is the value of *OscFlag*:

```

Time=218, Signals: [0 1 0 1 1 0 1 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1] [0]
Time=219, Signals: [1 1 0 1 1 0 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
Time=220, Signals: [0 0 1 1 1 0 1 1] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
Time=221, Signals: [1 0 1 1 1 0 1 1] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
Time=222, Signals: [0 1 1 1 1 0 1 1] [1 0 1 1 1 1 1 0 0 1 1 0 1] [0]
Time=223, Signals: [1 1 1 1 1 0 1 1] [1 0 0 1 1 1 0 1 0 0 0 1 1 1] [1]
Time=224, Signals: [0 0 0 0 1 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
Time=225, Signals: [1 0 0 0 1 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
Time=226, Signals: [0 1 0 0 1 1 1] [1 0 1 1 1 0 0 1 1 0 0 0 1] [0]
Time=227, Signals: [1 1 0 0 1 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]

```

Figure 13: Final Result

The final circuit with predicting function is shown below:

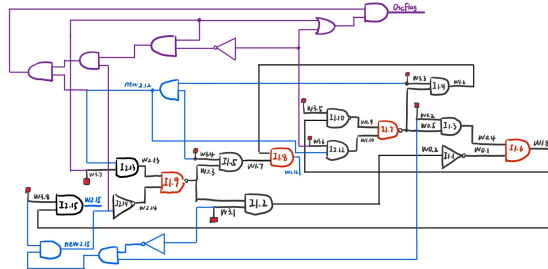


Figure 14: Final Circuit with Predicting Function

3 Generalized Solution

In section 1 and 2, we obtain a powerful circuit without oscillation possibility, while maintaining the same function as the original circuit and equipped with the predicting function. Despite the success in outputting the right result, we try to give a more generalized solution, which can be applied to circuits with various structures and sizes.

3.1 Circuit Topology Analysis

Apparently, a logic function is entailed to precisely describe the relationship between input wires and our target wire. We should realize one important point: not all the input wires are needed when building the logic function. Consequently, before the logic function simplification step in the next subsection, we try to minimize the number of inputs involved because it will lead to an exponential growth in the possible scenarios of logical functions. To do this, we analyze the topology of circuit following the designed algorithm flow.

For cutting off wires (like requirement 1 and 2), we can adopt the flow below:

Algorithm 1: Algorithm for Cutting off Wires

Input: Input wires I_1, I_2, \dots, I_n
Output: Logic Function F_w
 Use Verisim to get simulation result;
 Construct a Priority List for input wires based on their distance to the target wire (when the distance equals, arrange them in ASCII code character order);
 $i = 0, F_0 = \text{none}$;
while True **do**
 Add next input wire I_i from the top of Priority List into current logic function $F_{i-1}(I_1, I_2, \dots, I_{i-1})$;
 Construct and minimize F_i ;
 if F_i can satisfy the simulation result **then**
 $F_w = F_i$;
 break;
 else
 $i++$;
 end if
end while

Now we explain the algorithm flow in the following example: as figure 15 shows, the purple wire w_002_012 is the target wire, so the first priority in the Priority List is w_003_003 , and then w_003_003 , which are the closest two input wires to the target wire (drawn in red). Searching backwards, the following priority will belong to w_003_005 , w_003_006 and w_003_007 , which are drawn in blue.

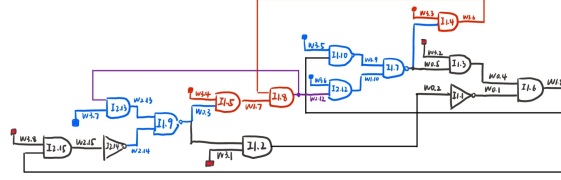


Figure 15: Example for Cutting off Wires

Next, we design a similar algorithm for finding the minimum inputs for the logic function of *OscFlag*:

Algorithm 2: Algorithm for *OscFlag*

Input: Input wires I_1, I_2, \dots, I_n

Output: Logic Function F_o

Use Verisim to get simulation result;

Find gates with multiple fanouts or located in the intersection of positive loops (core gates);

Construct a Priority List for input wires based on their distance to the core gates (when the distance equals, arrange them in ASCII code character order);

$i = 0, F_0 = \text{none}$;

while True **do**

 Add next input wire I_i from the top of Priority List into current logic function $F_{i-1}(I_1, I_2, \dots, I_{i-1})$;

 Construct and minimize F_i ;

if F_i can satisfy the simulation result **then**

$F_o = F_i$;

break;

else

$i++$;

end if

end while

We can demonstrate the algorithm flow in the following example: as figure 16 shows, first we find core gates, which are the gates with multiple fanouts or located in the intersection of positive loops, and they are drawn in red. Next, similar to the algorithm for cutting off wires, we construct Priority List based on the distance to core gates. The first tier in the Priority List includes the input wires within dashed boxes: w_003_003 , w_003_004 , w_003_005 , w_003_006 and w_003_007 .

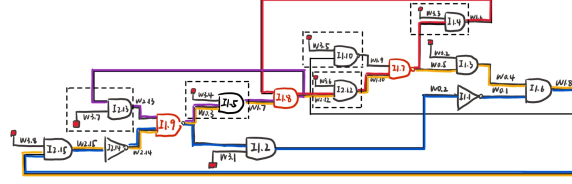


Figure 16: Example for *OscFlag*

Actually, we can refer to the logic functions we construct in *result5.v*:

```

1 assign new_w_002_012 = w_003_003 & w_003_004;
2 assign new_w_002_015 = ~w_003_001 & w_003_002 & w_003_008
;
3 assign OscFlag = w_003_003 & w_003_004 & (w_003_006 |
w_003_007) & ~(~w_003_001 & w_003_002 & ~w_003_006 &
w_003_007 & w_003_008);

```

Obviously, these logic functions involve a fraction of input wires only, rather than all of them, which confirms our theorem.

3.2 Logic Function Construction and Minimization

As the flow above shows, the step of logic function construction and minimization is the key to the algorithm, whose efficiency mainly accounts for the overall performance. So we should really emphasize its implementation.

Because the number of inputs n is finite, $k(\leq 2^n)$ effective input-output pairs can be always completely listed as a LUT. According to this LUT, the output can be definitely represented as the sum of minterms. Next, with the assistance of some mature algorithm, such as Quine-McCluskey [1] and ESPRESSO [2], the logic function can be effectively minimized.

Finally, we will obtain desired logic functions with conciseness, which can be implemented efficiently by fewer gates.

References

- [1] McCluskey, E. J. "Minimization of Boolean Functions*." Bell System Technical Journal, vol. 35, no. 6, Nov. 1956, pp. 1417–44. <https://doi.org/10.1002/j.1538-7305.1956.tb03835.x>.
- [2] McGeer, Patrick, et al. "ESPRESSO-SIGNATURE: A new exact minimizer for logic functions." Proceedings of the 30th international design automation conference. 1993.

A Appendix A: Standard Result (simulation of Q5_testcase.v)

```

Time= 0, Signals: [0 0 0 0 0 0 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 1, Signals: [1 0 0 0 0 0 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 2, Signals: [0 1 0 0 0 0 0 0] [1 0 1 1 1 0 0 1 1 0 0 0 1 0]
Time= 3, Signals: [1 1 0 0 0 0 0 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
Time= 4, Signals: [0 0 1 0 0 0 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 5, Signals: [1 0 1 0 0 0 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 6, Signals: [0 1 1 0 0 0 0 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0]
Time= 7, Signals: [1 1 1 0 0 0 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
Time= 8, Signals: [0 0 0 1 0 0 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 9, Signals: [1 0 0 1 0 0 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 10, Signals: [0 1 0 1 0 0 0 0] [1 0 1 1 1 1 0 1 1 1 0 0 0 1 0]
Time= 11, Signals: [1 1 0 1 0 0 0 0] [0 1 1 1 1 1 0 1 0 1 0 0 0 1 0]
Time= 12, Signals: [0 0 1 1 0 0 0 0] [1 0 1 0 1 1 1 1 0 1 0 1 0 1 0]
Time= 13, Signals: [1 0 1 1 0 0 0 0] [0 1 1 0 1 1 1 1 0 1 0 1 0 1 0]
Time= 14, Signals: [0 1 1 1 0 0 0 0] [1 0 1 1 1 1 1 1 1 0 1 0 1 0 1]
Time= 15, Signals: [1 1 1 1 0 0 0 0] [0 1 1 1 1 1 1 1 0 1 0 1 0 1 0]
Time= 16, Signals: [0 0 0 0 1 0 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 17, Signals: [1 0 0 0 1 0 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 18, Signals: [0 1 0 0 1 0 0 0] [1 0 1 1 1 1 0 0 1 0 0 0 0 1 0]
Time= 19, Signals: [1 1 0 0 1 0 0 0] [0 1 1 1 1 1 0 0 0 1 0 0 0 1 0]
Time= 20, Signals: [0 0 1 0 1 0 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 21, Signals: [1 0 1 0 1 0 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 22, Signals: [0 1 1 0 1 0 0 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0]
Time= 23, Signals: [1 1 1 0 1 0 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
Time= 24, Signals: [0 0 0 1 1 0 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 25, Signals: [1 0 0 1 1 0 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 26, Signals: [0 1 0 1 1 0 0 0] [1 0 1 1 1 1 0 1 1 0 0 0 0 1 0]
Time= 27, Signals: [1 1 0 1 1 0 0 0] [0 1 1 1 1 1 0 1 0 1 0 0 0 1 0]
Time= 28, Signals: [0 0 1 1 1 0 0 0] [1 0 1 0 1 1 1 1 0 1 0 1 0 1 0]
Time= 29, Signals: [1 0 1 1 1 0 0 0] [0 1 1 0 1 1 1 1 0 1 0 1 0 1 0]
Time= 30, Signals: [0 1 1 1 1 0 0 0] [1 0 1 1 1 1 1 1 1 0 0 1 0 1 0]
Time= 31, Signals: [1 1 1 1 1 0 0 0] [0 1 1 1 1 1 1 1 0 1 0 1 0 1 0]
Time= 32, Signals: [0 0 0 0 0 1 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 33, Signals: [1 0 0 0 0 1 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
Time= 34, Signals: [0 1 0 0 0 1 0 0] [1 0 1 1 1 1 0 0 1 1 0 0 0 1 0]
Time= 35, Signals: [1 1 0 0 0 1 0 0] [0 1 1 1 1 1 0 0 0 1 0 0 0 1 0]
Time= 36, Signals: [0 0 1 0 0 1 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 37, Signals: [1 0 1 0 0 1 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
Time= 38, Signals: [0 1 1 0 0 1 0 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0]
Time= 39, Signals: [1 1 1 0 0 1 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
Time= 40, Signals: [0 0 0 1 0 1 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
Time= 41, Signals: [1 0 0 1 0 1 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]

```

Time= 42, Signals: [0 1 0 1 0 1 0 0] [1 0 1 1 1 0 1 1 1 0 0 0 1 0]
 Time= 43, Signals: [1 1 0 1 0 1 0 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time= 44, Signals: [0 0 1 1 0 1 0 0] [1 0 1 0 x x 1 0 1 x x 0 1 0]
 Time= 45, Signals: [1 0 1 1 0 1 0 0] [0 1 1 0 x x 1 0 1 x x 0 1 0]
 Time= 46, Signals: [0 1 1 1 0 1 0 0] [1 0 1 x x x 1 x 1 x x 0 1 0]
 Time= 47, Signals: [1 1 1 1 0 1 0 0] [0 1 1 x x x 1 0 1 x x 0 1 0]
 Time= 48, Signals: [0 0 0 0 1 1 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 49, Signals: [1 0 0 0 1 1 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 50, Signals: [0 1 0 0 1 1 0 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0]
 Time= 51, Signals: [1 1 0 0 1 1 0 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time= 52, Signals: [0 0 1 0 1 1 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time= 53, Signals: [1 0 1 0 1 1 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time= 54, Signals: [0 1 1 0 1 1 0 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0]
 Time= 55, Signals: [1 1 1 0 1 1 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time= 56, Signals: [0 0 0 1 1 1 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time= 57, Signals: [1 0 0 1 1 1 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time= 58, Signals: [0 1 0 1 1 1 0 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0]
 Time= 59, Signals: [1 1 0 1 1 1 0 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time= 60, Signals: [0 0 1 1 1 1 0 0] [1 0 1 0 x x 1 0 1 x x 0 1 0]
 Time= 61, Signals: [1 0 1 1 1 1 0 0] [0 1 1 0 x x 1 0 1 x x 0 1 0]
 Time= 62, Signals: [0 1 1 1 1 1 0 0] [1 0 1 x x x 1 x x x x 0 1 0]
 Time= 63, Signals: [1 1 1 1 1 1 0 0] [0 1 1 x x x 1 0 1 x x 0 1 0]
 Time= 64, Signals: [0 0 0 0 0 0 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 65, Signals: [1 0 0 0 0 0 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 66, Signals: [0 1 0 0 0 0 1 0] [1 0 1 1 1 0 0 1 1 0 0 0 1 0]
 Time= 67, Signals: [1 1 0 0 0 0 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time= 68, Signals: [0 0 1 0 0 0 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time= 69, Signals: [1 0 1 0 0 0 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time= 70, Signals: [0 1 1 0 0 0 1 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0]
 Time= 71, Signals: [1 1 1 0 0 0 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time= 72, Signals: [0 0 0 1 0 0 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time= 73, Signals: [1 0 0 1 0 0 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time= 74, Signals: [0 1 0 1 0 0 1 0] [1 0 1 1 1 0 1 1 1 0 0 0 1 0]
 Time= 75, Signals: [1 1 0 1 0 0 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time= 76, Signals: [0 0 1 1 0 0 1 0] [1 0 x 0 1 1 x 0 1 0 x x 1 0]
 Time= 77, Signals: [1 0 1 1 0 0 1 0] [x x x 0 1 1 x 0 1 0 x x 1 0]
 Time= 78, Signals: [0 1 1 1 0 0 1 0] [1 0 x 1 1 1 x 1 1 0 x x 1 0]
 Time= 79, Signals: [1 1 1 1 0 0 1 0] [x x x 1 1 1 x x 1 0 x x 1 0]
 Time= 80, Signals: [0 0 0 0 1 0 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 81, Signals: [1 0 0 0 1 0 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 82, Signals: [0 1 0 0 1 0 1 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0]
 Time= 83, Signals: [1 1 0 0 1 0 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time= 84, Signals: [0 0 1 0 1 0 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time= 85, Signals: [1 0 1 0 1 0 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time= 86, Signals: [0 1 1 0 1 0 1 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0]
 Time= 87, Signals: [1 1 1 0 1 0 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]

Time= 88, Signals: [0 0 0 1 1 0 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time= 89, Signals: [1 0 0 1 1 0 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time= 90, Signals: [0 1 0 1 1 0 1 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0]
 Time= 91, Signals: [1 1 0 1 1 0 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time= 92, Signals: [0 0 1 1 1 0 1 0] [1 0 x 0 1 1 x 0 1 0 x x 1 0]
 Time= 93, Signals: [1 0 1 1 1 0 1 0] [x x x 0 1 1 x 0 1 0 x x 1 0]
 Time= 94, Signals: [0 1 1 1 1 0 1 0] [1 0 x 1 1 1 x 1 0 0 x x 1 0]
 Time= 95, Signals: [1 1 1 1 1 0 1 0] [x x x 1 1 1 x x x 0 x x 1 0]
 Time= 96, Signals: [0 0 0 0 1 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 97, Signals: [1 0 0 0 1 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time= 98, Signals: [0 1 0 0 1 1 0] [1 0 1 1 1 0 0 1 1 0 0 0 1 0]
 Time= 99, Signals: [1 1 0 0 1 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=100, Signals: [0 0 1 0 0 1 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=101, Signals: [1 0 1 0 0 1 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=102, Signals: [0 1 1 0 0 1 1 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0]
 Time=103, Signals: [1 1 1 0 0 1 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=104, Signals: [0 0 0 1 0 1 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=105, Signals: [1 0 0 1 0 1 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=106, Signals: [0 1 0 1 0 1 1 0] [1 0 1 1 1 0 1 1 1 0 0 0 1 0]
 Time=107, Signals: [1 1 0 1 0 1 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=108, Signals: [0 0 1 1 0 1 1 0] [1 0 x 0 x x x 0 1 x x x 1 0]
 Time=109, Signals: [1 0 1 1 0 1 1 0] [x x x 0 x x x 0 1 x x x 1 0]
 Time=110, Signals: [0 1 1 1 0 1 1 0] [1 0 x x x x x x 1 x x x 1 0]
 Time=111, Signals: [1 1 1 1 0 1 1 0] [x x x x x x x x 1 x x x 1 0]
 Time=112, Signals: [0 0 0 0 1 1 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=113, Signals: [1 0 0 0 1 1 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=114, Signals: [0 1 0 0 1 1 1 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0]
 Time=115, Signals: [1 1 0 0 1 1 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=116, Signals: [0 0 1 0 1 1 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=117, Signals: [1 0 1 0 1 1 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=118, Signals: [0 1 1 0 1 1 1 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0]
 Time=119, Signals: [1 1 1 0 1 1 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=120, Signals: [0 0 0 1 1 1 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=121, Signals: [1 0 0 1 1 1 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=122, Signals: [0 1 0 1 1 1 1 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0]
 Time=123, Signals: [1 1 0 1 1 1 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=124, Signals: [0 0 1 1 1 1 1 0] [1 0 x 0 x x x 0 1 x x x 1 0]
 Time=125, Signals: [1 0 1 1 1 1 1 0] [x x x 0 x x x 0 1 x x x 1 0]
 Time=126, Signals: [0 1 1 1 1 1 1 0] [1 0 x x x x x x x x x x 1 0]
 Time=127, Signals: [1 1 1 1 1 1 1 0] [x x x x x x x x x x x x 1 0]
 Time=128, Signals: [0 0 0 0 0 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=129, Signals: [1 0 0 0 0 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=130, Signals: [0 1 0 0 0 0 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1]
 Time=131, Signals: [1 1 0 0 0 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=132, Signals: [0 0 1 0 0 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=133, Signals: [1 0 1 0 0 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]

Time=134, Signals: [0 1 1 0 0 0 0 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1]
 Time=135, Signals: [1 1 1 0 0 0 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=136, Signals: [0 0 0 1 0 0 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=137, Signals: [1 0 0 1 0 0 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=138, Signals: [0 1 0 1 0 0 0 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1]
 Time=139, Signals: [1 1 0 1 0 0 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=140, Signals: [0 0 1 1 0 0 0 1] [1 0 1 0 1 1 1 0 1 0 1 0 1 0]
 Time=141, Signals: [1 0 1 1 0 0 0 1] [0 1 1 0 1 1 1 0 1 0 1 0 1 0]
 Time=142, Signals: [0 1 1 1 0 0 0 1] [1 0 1 1 1 1 1 1 1 0 1 0 0 1]
 Time=143, Signals: [1 1 1 1 0 0 0 1] [0 1 1 1 1 1 1 0 1 0 1 0 1 0]
 Time=144, Signals: [0 0 0 0 1 0 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=145, Signals: [1 0 0 0 1 0 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=146, Signals: [0 1 0 0 1 0 0 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1]
 Time=147, Signals: [1 1 0 0 1 0 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=148, Signals: [0 0 1 0 1 0 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=149, Signals: [1 0 1 0 1 0 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=150, Signals: [0 1 1 0 1 0 0 1] [1 0 1 1 1 1 0 1 0 0 0 0 0 1]
 Time=151, Signals: [1 1 1 0 1 0 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=152, Signals: [0 0 0 1 1 0 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=153, Signals: [1 0 0 1 1 0 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=154, Signals: [0 1 0 1 1 0 0 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1]
 Time=155, Signals: [1 1 0 1 1 0 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=156, Signals: [0 0 1 1 1 0 0 1] [1 0 1 0 1 1 1 0 1 0 1 0 1 0]
 Time=157, Signals: [1 0 1 1 1 0 0 1] [0 1 1 0 1 1 1 0 1 0 1 0 1 0]
 Time=158, Signals: [0 1 1 1 1 0 0 1] [1 0 1 1 1 1 1 1 0 0 1 0 0 1]
 Time=159, Signals: [1 1 1 1 1 0 0 1] [0 1 1 1 1 1 1 0 1 0 1 0 1 0]
 Time=160, Signals: [0 0 0 0 0 1 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=161, Signals: [1 0 0 0 0 1 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=162, Signals: [0 1 0 0 0 1 0 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1]
 Time=163, Signals: [1 1 0 0 0 1 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=164, Signals: [0 0 1 0 0 1 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=165, Signals: [1 0 1 0 0 1 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=166, Signals: [0 1 1 0 0 1 0 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1]
 Time=167, Signals: [1 1 1 0 0 1 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=168, Signals: [0 0 0 1 0 1 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=169, Signals: [1 0 0 1 0 1 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=170, Signals: [0 1 0 1 0 1 0 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1]
 Time=171, Signals: [1 1 0 1 0 1 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=172, Signals: [0 0 1 1 0 1 0 1] [1 0 1 0 x x 1 0 1 x x 0 1 0]
 Time=173, Signals: [1 0 1 1 0 1 0 1] [0 1 1 0 x x 1 0 1 x x 0 1 0]
 Time=174, Signals: [0 1 1 1 0 1 0 1] [1 0 1 x x x 1 x 1 x x 0 x x]
 Time=175, Signals: [1 1 1 1 0 1 0 1] [0 1 1 x x x 1 0 1 x x 0 1 0]
 Time=176, Signals: [0 0 0 0 1 1 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=177, Signals: [1 0 0 0 1 1 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=178, Signals: [0 1 0 0 1 1 0 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1]
 Time=179, Signals: [1 1 0 0 1 1 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]

Time=180, Signals: [0 0 1 0 1 1 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=181, Signals: [1 0 1 0 1 1 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=182, Signals: [0 1 1 0 1 1 0 1] [1 0 1 1 1 1 0 1 0 0 0 0 1]
 Time=183, Signals: [1 1 1 0 1 1 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=184, Signals: [0 0 0 1 1 1 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=185, Signals: [1 0 0 1 1 1 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=186, Signals: [0 1 0 1 1 1 0 1] [1 0 1 1 1 0 1 1 0 0 0 0 1]
 Time=187, Signals: [1 1 0 1 1 1 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=188, Signals: [0 0 1 1 1 1 0 1] [1 0 1 0 x x 1 0 1 x x 0 1 0]
 Time=189, Signals: [1 0 1 1 1 1 0 1] [0 1 1 0 x x 1 0 1 x x 0 1 0]
 Time=190, Signals: [0 1 1 1 1 1 0 1] [1 0 1 x x x 1 x x x 0 x x]
 Time=191, Signals: [1 1 1 1 1 1 0 1] [0 1 1 x x x 1 0 1 x x 0 1 0]
 Time=192, Signals: [0 0 0 0 0 0 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=193, Signals: [1 0 0 0 0 0 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=194, Signals: [0 1 0 0 0 0 1 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1]
 Time=195, Signals: [1 1 0 0 0 0 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=196, Signals: [0 0 1 0 0 0 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=197, Signals: [1 0 1 0 0 0 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=198, Signals: [0 1 1 0 0 0 1 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1]
 Time=199, Signals: [1 1 1 0 0 0 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=200, Signals: [0 0 0 1 0 0 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=201, Signals: [1 0 0 1 0 0 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=202, Signals: [0 1 0 1 0 0 1 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1]
 Time=203, Signals: [1 1 0 1 0 0 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=204, Signals: [0 0 1 1 0 0 1 1] [1 0 x 0 1 1 x 0 1 0 x x 1 0]
 Time=205, Signals: [1 0 1 1 0 0 1 1] [x x x 0 1 1 x 0 1 0 x x 1 0]
 Time=206, Signals: [0 1 1 1 0 0 1 1] [1 0 1 1 1 1 1 1 1 0 1 1 0 1]
 Time=207, Signals: [1 1 1 1 0 0 1 1] [x x x 1 1 1 x x 1 0 x x x]
 Time=208, Signals: [0 0 0 0 1 0 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=209, Signals: [1 0 0 0 1 0 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=210, Signals: [0 1 0 0 1 0 1 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1]
 Time=211, Signals: [1 1 0 0 1 0 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=212, Signals: [0 0 1 0 1 0 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=213, Signals: [1 0 1 0 1 0 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=214, Signals: [0 1 1 0 1 0 1 1] [1 0 1 1 1 1 0 1 0 0 0 0 0 1]
 Time=215, Signals: [1 1 1 0 1 0 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=216, Signals: [0 0 0 1 1 0 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=217, Signals: [1 0 0 1 1 0 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=218, Signals: [0 1 0 1 1 0 1 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1]
 Time=219, Signals: [1 1 0 1 1 0 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=220, Signals: [0 0 1 1 1 0 1 1] [1 0 x 0 1 1 x 0 1 0 x x 1 0]
 Time=221, Signals: [1 0 1 1 1 0 1 1] [x x x 0 1 1 x 0 1 0 x x 1 0]
 Time=222, Signals: [0 1 1 1 1 0 1 1] [1 0 1 1 1 1 1 1 0 0 1 1 0 1]
 Time=223, Signals: [1 1 1 1 1 0 1 1] [x x x 1 1 1 x x x 0 x x x]
 Time=224, Signals: [0 0 0 0 0 1 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=225, Signals: [1 0 0 0 0 1 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]

Time=226, Signals: [0 1 0 0 0 1 1 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1]
 Time=227, Signals: [1 1 0 0 0 1 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=228, Signals: [0 0 1 0 0 1 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=229, Signals: [1 0 1 0 0 1 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=230, Signals: [0 1 1 0 0 1 1 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1]
 Time=231, Signals: [1 1 1 0 0 1 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=232, Signals: [0 0 0 1 0 1 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=233, Signals: [1 0 0 1 0 1 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=234, Signals: [0 1 0 1 0 1 1 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1]
 Time=235, Signals: [1 1 0 1 0 1 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=236, Signals: [0 0 1 1 0 1 1 1] [1 0 x 0 x x x 0 1 x x x 1 0]
 Time=237, Signals: [1 0 1 1 0 1 1 1] [x x x 0 x x x 0 1 x x x 1 0]
 Time=238, Signals: [0 1 1 1 0 1 1 1] [1 0 x x x x x x 1 x x x x x]
 Time=239, Signals: [1 1 1 1 0 1 1 1] [x x x x x x x x 1 x x x x x]
 Time=240, Signals: [0 0 0 0 1 1 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=241, Signals: [1 0 0 0 1 1 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0]
 Time=242, Signals: [0 1 0 0 1 1 1 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1]
 Time=243, Signals: [1 1 0 0 1 1 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0]
 Time=244, Signals: [0 0 1 0 1 1 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=245, Signals: [1 0 1 0 1 1 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0]
 Time=246, Signals: [0 1 1 0 1 1 1 1] [1 0 1 1 1 1 0 1 0 0 0 0 0 1]
 Time=247, Signals: [1 1 1 0 1 1 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0]
 Time=248, Signals: [0 0 0 1 1 1 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=249, Signals: [1 0 0 1 1 1 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0]
 Time=250, Signals: [0 1 0 1 1 1 1 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1]
 Time=251, Signals: [1 1 0 1 1 1 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0]
 Time=252, Signals: [0 0 1 1 1 1 1 1] [1 0 x 0 x x x 0 1 x x x 1 0]
 Time=253, Signals: [1 0 1 1 1 1 1 1] [x x x 0 x x x 0 1 x x x 1 0]
 Time=254, Signals: [0 1 1 1 1 1 1 1] [1 0 x x x x x x x x x x x x]
 Time=255, Signals: [1 1 1 1 1 1 1 1] [x x x x x x x x x x x x x x]

B Appendix B: Our Result (simulation of result5.v)

Time= 0, Signals: [0 0 0 0 0 0 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 1, Signals: [1 0 0 0 0 0 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 2, Signals: [0 1 0 0 0 0 0 0] [1 0 1 1 1 0 0 1 1 0 0 0 1 0] [0]
 Time= 3, Signals: [1 1 0 0 0 0 0 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 4, Signals: [0 0 1 0 0 0 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 5, Signals: [1 0 1 0 0 0 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 6, Signals: [0 1 1 0 0 0 0 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0] [0]
 Time= 7, Signals: [1 1 1 0 0 0 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 8, Signals: [0 0 0 1 0 0 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 9, Signals: [1 0 0 1 0 0 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]

Time= 10, Signals: [0 1 0 1 0 0 0 0] [1 0 1 1 1 0 1 1 1 0 0 0 1 0] [0]
 Time= 11, Signals: [1 1 0 1 0 0 0 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 12, Signals: [0 0 1 1 0 0 0 0] [1 0 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time= 13, Signals: [1 0 1 1 0 0 0 0] [0 1 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time= 14, Signals: [0 1 1 1 0 0 0 0] [1 0 1 1 1 1 1 1 1 0 1 0 1 0] [0]
 Time= 15, Signals: [1 1 1 1 0 0 0 0] [0 1 1 1 1 1 1 0 1 0 1 0 1 0] [0]
 Time= 16, Signals: [0 0 0 0 1 0 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 17, Signals: [1 0 0 0 1 0 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 18, Signals: [0 1 0 0 1 0 0 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0] [0]
 Time= 19, Signals: [1 1 0 0 1 0 0 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 20, Signals: [0 0 1 0 1 0 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 21, Signals: [1 0 1 0 1 0 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 22, Signals: [0 1 1 0 1 0 0 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0] [0]
 Time= 23, Signals: [1 1 1 0 1 0 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 24, Signals: [0 0 0 1 1 0 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 25, Signals: [1 0 0 1 1 0 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 26, Signals: [0 1 0 1 1 0 0 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0] [0]
 Time= 27, Signals: [1 1 0 1 1 0 0 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 28, Signals: [0 0 1 1 1 0 0 0] [1 0 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time= 29, Signals: [1 0 1 1 1 0 0 0] [0 1 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time= 30, Signals: [0 1 1 1 1 0 0 0] [1 0 1 1 1 1 1 1 0 0 1 0 1 0] [0]
 Time= 31, Signals: [1 1 1 1 1 0 0 0] [0 1 1 1 1 1 1 0 1 0 1 0 1 0] [0]
 Time= 32, Signals: [0 0 0 0 1 0 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 33, Signals: [1 0 0 0 1 0 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 34, Signals: [0 1 0 0 1 0 0 0] [1 0 1 1 1 0 0 1 1 0 0 0 1 0] [0]
 Time= 35, Signals: [1 1 0 0 1 0 0 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 36, Signals: [0 0 1 0 0 1 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 37, Signals: [1 0 1 0 0 1 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 38, Signals: [0 1 1 0 0 1 0 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0] [0]
 Time= 39, Signals: [1 1 1 0 0 1 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 40, Signals: [0 0 0 1 0 1 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 41, Signals: [1 0 0 1 0 1 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 42, Signals: [0 1 0 1 0 1 0 0] [1 0 1 1 1 0 1 1 1 0 0 0 1 0] [0]
 Time= 43, Signals: [1 1 0 1 0 1 0 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 44, Signals: [0 0 1 1 0 1 0 0] [1 0 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 45, Signals: [1 0 1 1 0 1 0 0] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 46, Signals: [0 1 1 1 0 1 0 0] [1 0 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 47, Signals: [1 1 1 1 0 1 0 0] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 48, Signals: [0 0 0 0 1 1 0 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 49, Signals: [1 0 0 0 1 1 0 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 50, Signals: [0 1 0 0 1 1 0 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0] [0]
 Time= 51, Signals: [1 1 0 0 1 1 0 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 52, Signals: [0 0 1 0 1 1 0 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 53, Signals: [1 0 1 0 1 1 0 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 54, Signals: [0 1 1 0 1 1 0 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0] [0]
 Time= 55, Signals: [1 1 1 0 1 1 0 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]

Time= 56, Signals: [0 0 0 1 1 1 0 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 57, Signals: [1 0 0 1 1 1 0 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 58, Signals: [0 1 0 1 1 1 0 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0] [0]
 Time= 59, Signals: [1 1 0 1 1 1 0 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 60, Signals: [0 0 1 1 1 1 0 0] [1 0 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 61, Signals: [1 0 1 1 1 1 0 0] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 62, Signals: [0 1 1 1 1 1 0 0] [1 0 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 63, Signals: [1 1 1 1 1 1 0 0] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time= 64, Signals: [0 0 0 0 0 0 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 65, Signals: [1 0 0 0 0 0 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 66, Signals: [0 1 0 0 0 0 1 0] [1 0 1 1 1 0 0 1 1 0 0 0 1 0] [0]
 Time= 67, Signals: [1 1 0 0 0 0 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 68, Signals: [0 0 1 0 0 0 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 69, Signals: [1 0 1 0 0 0 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 70, Signals: [0 1 1 0 0 0 1 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0] [0]
 Time= 71, Signals: [1 1 1 0 0 0 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 72, Signals: [0 0 0 1 0 0 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 73, Signals: [1 0 0 1 0 0 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 74, Signals: [0 1 0 1 0 0 1 0] [1 0 1 1 1 0 1 1 1 0 0 0 1 0] [0]
 Time= 75, Signals: [1 1 0 1 0 0 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 76, Signals: [0 0 1 1 0 0 1 0] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time= 77, Signals: [1 0 1 1 0 0 1 0] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time= 78, Signals: [0 1 1 1 0 0 1 0] [1 0 0 1 1 1 0 1 1 0 0 1 1 0] [1]
 Time= 79, Signals: [1 1 1 1 0 0 1 0] [1 0 0 1 1 1 0 1 1 0 0 1 1 0] [1]
 Time= 80, Signals: [0 0 0 0 1 0 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 81, Signals: [1 0 0 0 1 0 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 82, Signals: [0 1 0 0 1 0 1 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0] [0]
 Time= 83, Signals: [1 1 0 0 1 0 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 84, Signals: [0 0 1 0 1 0 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 85, Signals: [1 0 1 0 1 0 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 86, Signals: [0 1 1 0 1 0 1 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0] [0]
 Time= 87, Signals: [1 1 1 0 1 0 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time= 88, Signals: [0 0 0 1 1 0 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 89, Signals: [1 0 0 1 1 0 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 90, Signals: [0 1 0 1 1 0 1 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0] [0]
 Time= 91, Signals: [1 1 0 1 1 0 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time= 92, Signals: [0 0 1 1 1 0 1 0] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time= 93, Signals: [1 0 1 1 1 0 1 0] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time= 94, Signals: [0 1 1 1 1 0 1 0] [1 0 0 1 1 1 0 1 0 0 0 1 1 0] [1]
 Time= 95, Signals: [1 1 1 1 1 0 1 0] [1 0 0 1 1 1 0 1 0 0 0 1 1 0] [1]
 Time= 96, Signals: [0 0 0 0 0 1 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 97, Signals: [1 0 0 0 0 1 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time= 98, Signals: [0 1 0 0 0 1 1 0] [1 0 1 1 1 0 0 1 1 0 0 0 1 0] [0]
 Time= 99, Signals: [1 1 0 0 0 1 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=100, Signals: [0 0 1 0 0 1 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=101, Signals: [1 0 1 0 0 1 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]

Time=102, Signals: [0 1 1 0 0 1 1 0] [1 0 1 1 1 1 0 1 1 0 0 0 1 0] [0]
 Time=103, Signals: [1 1 1 0 0 1 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=104, Signals: [0 0 0 1 0 1 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=105, Signals: [1 0 0 1 0 1 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=106, Signals: [0 1 0 1 0 1 1 0] [1 0 1 1 1 0 1 1 1 0 0 0 1 0] [0]
 Time=107, Signals: [1 1 0 1 0 1 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=108, Signals: [0 0 1 1 0 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=109, Signals: [1 0 1 1 0 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=110, Signals: [0 1 1 1 0 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=111, Signals: [1 1 1 1 0 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=112, Signals: [0 0 0 0 1 1 1 0] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=113, Signals: [1 0 0 0 1 1 1 0] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=114, Signals: [0 1 0 0 1 1 1 0] [1 0 1 1 1 0 0 1 0 0 0 0 1 0] [0]
 Time=115, Signals: [1 1 0 0 1 1 1 0] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=116, Signals: [0 0 1 0 1 1 1 0] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=117, Signals: [1 0 1 0 1 1 1 0] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=118, Signals: [0 1 1 0 1 1 1 0] [1 0 1 1 1 1 0 1 0 0 0 0 1 0] [0]
 Time=119, Signals: [1 1 1 0 1 1 1 0] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=120, Signals: [0 0 0 1 1 1 1 0] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=121, Signals: [1 0 0 1 1 1 1 0] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=122, Signals: [0 1 0 1 1 1 1 0] [1 0 1 1 1 0 1 1 0 0 0 0 1 0] [0]
 Time=123, Signals: [1 1 0 1 1 1 1 0] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=124, Signals: [0 0 1 1 1 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=125, Signals: [1 0 1 1 1 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=126, Signals: [0 1 1 1 1 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=127, Signals: [1 1 1 1 1 1 1 0] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=128, Signals: [0 0 0 0 0 0 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=129, Signals: [1 0 0 0 0 0 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=130, Signals: [0 1 0 0 0 0 0 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1] [0]
 Time=131, Signals: [1 1 0 0 0 0 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=132, Signals: [0 0 1 0 0 0 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=133, Signals: [1 0 1 0 0 0 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=134, Signals: [0 1 1 0 0 0 0 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1] [0]
 Time=135, Signals: [1 1 1 0 0 0 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=136, Signals: [0 0 0 1 0 0 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=137, Signals: [1 0 0 1 0 0 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=138, Signals: [0 1 0 1 0 0 0 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1] [0]
 Time=139, Signals: [1 1 0 1 0 0 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=140, Signals: [0 0 1 1 0 0 0 1] [1 0 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time=141, Signals: [1 0 1 1 0 0 0 1] [0 1 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time=142, Signals: [0 1 1 1 0 0 0 1] [1 0 1 1 1 1 1 1 1 0 1 0 0 1] [0]
 Time=143, Signals: [1 1 1 1 0 0 0 1] [0 1 1 1 1 1 1 0 1 0 1 0 1 0] [0]
 Time=144, Signals: [0 0 0 0 1 0 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=145, Signals: [1 0 0 0 1 0 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=146, Signals: [0 1 0 0 1 0 0 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1] [0]
 Time=147, Signals: [1 1 0 0 1 0 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]

Time=148, Signals: [0 0 1 0 1 0 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=149, Signals: [1 0 1 0 1 0 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=150, Signals: [0 1 1 0 1 0 0 1] [1 0 1 1 1 1 0 1 0 0 0 0 1] [0]
 Time=151, Signals: [1 1 1 0 1 0 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=152, Signals: [0 0 0 1 1 0 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=153, Signals: [1 0 0 1 1 0 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=154, Signals: [0 1 0 1 1 0 0 1] [1 0 1 1 1 0 1 1 0 0 0 0 1] [0]
 Time=155, Signals: [1 1 0 1 1 0 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=156, Signals: [0 0 1 1 1 0 0 1] [1 0 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time=157, Signals: [1 0 1 1 1 0 0 1] [0 1 1 0 1 1 1 0 1 0 1 0 1 0] [0]
 Time=158, Signals: [0 1 1 1 1 0 0 1] [1 0 1 1 1 1 1 1 0 0 1 0 0 1] [0]
 Time=159, Signals: [1 1 1 1 1 0 0 1] [0 1 1 1 1 1 1 0 1 0 1 0 1 0] [0]
 Time=160, Signals: [0 0 0 0 0 1 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=161, Signals: [1 0 0 0 0 1 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=162, Signals: [0 1 0 0 0 1 0 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1] [0]
 Time=163, Signals: [1 1 0 0 0 1 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=164, Signals: [0 0 1 0 0 1 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=165, Signals: [1 0 1 0 0 1 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=166, Signals: [0 1 1 0 0 1 0 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1] [0]
 Time=167, Signals: [1 1 1 0 0 1 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=168, Signals: [0 0 0 1 0 1 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=169, Signals: [1 0 0 1 0 1 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=170, Signals: [0 1 0 1 0 1 0 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1] [0]
 Time=171, Signals: [1 1 0 1 0 1 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=172, Signals: [0 0 1 1 0 1 0 1] [1 0 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time=173, Signals: [1 0 1 1 0 1 0 1] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time=174, Signals: [0 1 1 1 0 1 0 1] [1 0 1 0 0 0 1 0 1 1 0 0 0 0] [1]
 Time=175, Signals: [1 1 1 1 0 1 0 1] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time=176, Signals: [0 0 0 0 1 1 0 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=177, Signals: [1 0 0 0 1 1 0 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=178, Signals: [0 1 0 0 1 1 0 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1] [0]
 Time=179, Signals: [1 1 0 0 1 1 0 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=180, Signals: [0 0 1 0 1 1 0 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=181, Signals: [1 0 1 0 1 1 0 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=182, Signals: [0 1 1 0 1 1 0 1] [1 0 1 1 1 1 0 1 0 0 0 0 0 1] [0]
 Time=183, Signals: [1 1 1 0 1 1 0 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=184, Signals: [0 0 0 1 1 1 0 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=185, Signals: [1 0 0 1 1 1 0 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=186, Signals: [0 1 0 1 1 1 0 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1] [0]
 Time=187, Signals: [1 1 0 1 1 1 0 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=188, Signals: [0 0 1 1 1 1 0 1] [1 0 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time=189, Signals: [1 0 1 1 1 1 0 1] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time=190, Signals: [0 1 1 1 1 1 0 1] [1 0 1 0 0 0 1 0 1 1 0 0 0 0] [1]
 Time=191, Signals: [1 1 1 1 1 1 0 1] [0 1 1 0 0 0 1 0 1 1 0 0 1 0] [1]
 Time=192, Signals: [0 0 0 0 0 0 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=193, Signals: [1 0 0 0 0 0 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]

Time=194, Signals: [0 1 0 0 0 0 1 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1] [0]
 Time=195, Signals: [1 1 0 0 0 0 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=196, Signals: [0 0 1 0 0 0 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=197, Signals: [1 0 1 0 0 0 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=198, Signals: [0 1 1 0 0 0 1 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1] [0]
 Time=199, Signals: [1 1 1 0 0 0 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=200, Signals: [0 0 0 1 0 0 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=201, Signals: [1 0 0 1 0 0 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=202, Signals: [0 1 0 1 0 0 1 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1] [0]
 Time=203, Signals: [1 1 0 1 0 0 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=204, Signals: [0 0 1 1 0 0 1 1] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time=205, Signals: [1 0 1 1 0 0 1 1] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time=206, Signals: [0 1 1 1 0 0 1 1] [1 0 1 1 1 1 1 1 1 0 1 1 0 1] [0]
 Time=207, Signals: [1 1 1 1 0 0 1 1] [1 0 0 1 1 1 0 1 1 0 0 1 1 1] [1]
 Time=208, Signals: [0 0 0 0 1 0 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=209, Signals: [1 0 0 0 1 0 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=210, Signals: [0 1 0 0 1 0 1 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1] [0]
 Time=211, Signals: [1 1 0 0 1 0 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=212, Signals: [0 0 1 0 1 0 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=213, Signals: [1 0 1 0 1 0 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=214, Signals: [0 1 1 0 1 0 1 1] [1 0 1 1 1 1 0 1 0 0 0 0 0 1] [0]
 Time=215, Signals: [1 1 1 0 1 0 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=216, Signals: [0 0 0 1 1 0 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=217, Signals: [1 0 0 1 1 0 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=218, Signals: [0 1 0 1 1 0 1 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1] [0]
 Time=219, Signals: [1 1 0 1 1 0 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=220, Signals: [0 0 1 1 1 0 1 1] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time=221, Signals: [1 0 1 1 1 0 1 1] [1 0 0 0 1 1 0 0 1 0 0 1 1 0] [1]
 Time=222, Signals: [0 1 1 1 1 0 1 1] [1 0 1 1 1 1 1 1 0 0 1 1 0 1] [0]
 Time=223, Signals: [1 1 1 1 1 0 1 1] [1 0 0 1 1 1 0 1 0 0 0 1 1 1] [1]
 Time=224, Signals: [0 0 0 0 0 1 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=225, Signals: [1 0 0 0 0 1 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=226, Signals: [0 1 0 0 0 1 1 1] [1 0 1 1 1 0 0 1 1 0 0 0 0 1] [0]
 Time=227, Signals: [1 1 0 0 0 1 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=228, Signals: [0 0 1 0 0 1 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=229, Signals: [1 0 1 0 0 1 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=230, Signals: [0 1 1 0 0 1 1 1] [1 0 1 1 1 1 0 1 1 0 0 0 0 1] [0]
 Time=231, Signals: [1 1 1 0 0 1 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=232, Signals: [0 0 0 1 0 1 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=233, Signals: [1 0 0 1 0 1 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=234, Signals: [0 1 0 1 0 1 1 1] [1 0 1 1 1 0 1 1 1 0 0 0 0 1] [0]
 Time=235, Signals: [1 1 0 1 0 1 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=236, Signals: [0 0 1 1 0 1 1 1] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=237, Signals: [1 0 1 1 0 1 1 1] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=238, Signals: [0 1 1 1 0 1 1 1] [1 0 1 0 0 0 1 0 1 1 0 1 0 0] [1]
 Time=239, Signals: [1 1 1 1 0 1 1 1] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]

Time=240, Signals: [0 0 0 0 1 1 1 1] [1 0 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=241, Signals: [1 0 0 0 1 1 1 1] [0 1 1 0 1 0 0 0 1 0 0 0 1 0] [0]
 Time=242, Signals: [0 1 0 0 1 1 1 1] [1 0 1 1 1 0 0 1 0 0 0 0 0 1] [0]
 Time=243, Signals: [1 1 0 0 1 1 1 1] [0 1 1 1 1 0 0 0 1 0 0 0 1 0] [0]
 Time=244, Signals: [0 0 1 0 1 1 1 1] [1 0 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=245, Signals: [1 0 1 0 1 1 1 1] [0 1 1 0 1 1 0 0 1 0 0 0 1 0] [0]
 Time=246, Signals: [0 1 1 0 1 1 1 1] [1 0 1 1 1 1 0 1 0 0 0 0 0 1] [0]
 Time=247, Signals: [1 1 1 0 1 1 1 1] [0 1 1 1 1 1 0 0 1 0 0 0 1 0] [0]
 Time=248, Signals: [0 0 0 1 1 1 1 1] [1 0 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=249, Signals: [1 0 0 1 1 1 1 1] [0 1 1 0 1 0 1 0 1 0 0 0 1 0] [0]
 Time=250, Signals: [0 1 0 1 1 1 1 1] [1 0 1 1 1 0 1 1 0 0 0 0 0 1] [0]
 Time=251, Signals: [1 1 0 1 1 1 1 1] [0 1 1 1 1 0 1 0 1 0 0 0 1 0] [0]
 Time=252, Signals: [0 0 1 1 1 1 1 1] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=253, Signals: [1 0 1 1 1 1 1 1] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]
 Time=254, Signals: [0 1 1 1 1 1 1 1] [1 0 1 0 0 0 1 0 1 1 0 1 0 0] [1]
 Time=255, Signals: [1 1 1 1 1 1 1 1] [1 0 0 0 0 0 0 0 1 1 0 1 1 0] [1]